

Interconnections and Signal Integrity

José Schutt-Ainé
SemChip

DAC Tutorial

22, June 2001

DAC 2001

© SEMCHIP

1

Future System Needs and Functions


Auto



Digital Wireless



Analog, RF
Computer

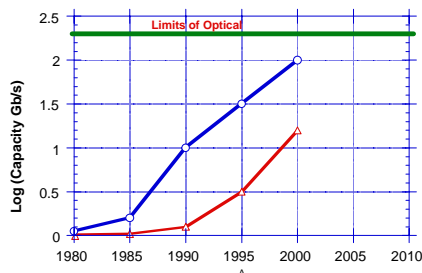

High-speed Digital


DAC 2001

High bandwidth

© SEMCHIP

2

The Interconnect Bottleneck

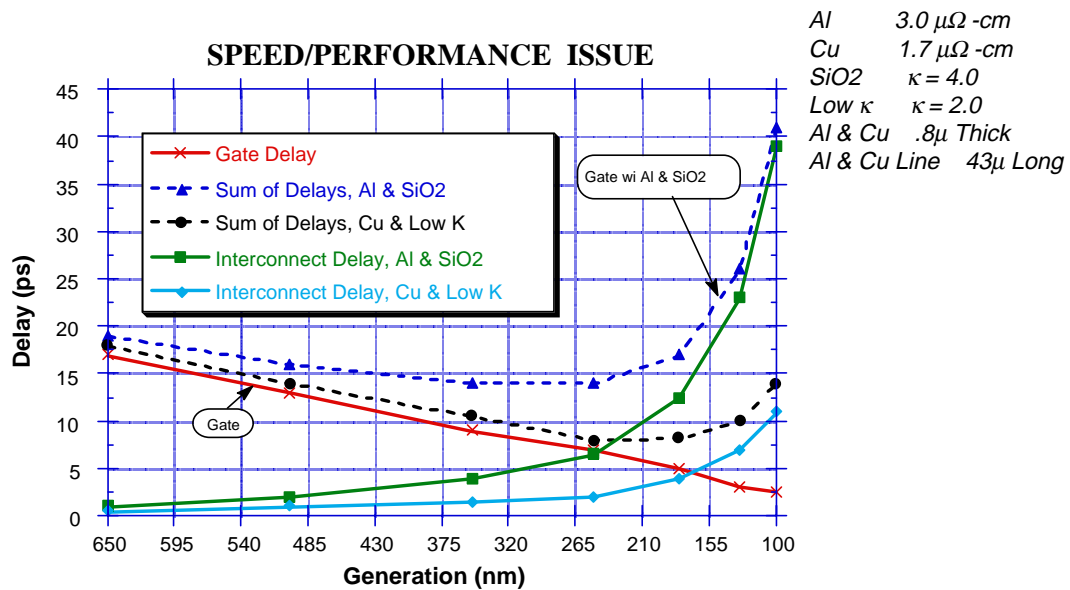

DAC 2001

© SEMCHIP

3

Semiconductor Technology Trends

	1997	2003	2006	2012
Chip size (mm ²)	300	430	520	750
Number of transistors (million)	11	76	200	1400
Interconnect width (nm)	200	100	70	35
Total interconnect length (km)	2.16	2.84	5.14	24

DAC 2001


© SEMCHIP

4

The Interconnect Bottleneck

Technology Generation	MOSFET Intrinsic Switching Delay	Response Time
1.0 μm	~ 10 ps	~ 1 ps
0.01 μm	~ 1 ps	~ 100 ps

Chip-Level Interconnect Delay


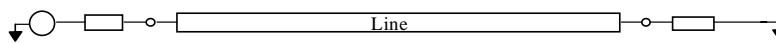


Pulse Characteristics:

rise time: 100 ps
fall time: 100 ps
pulse width: 4ns

Line Characteristics

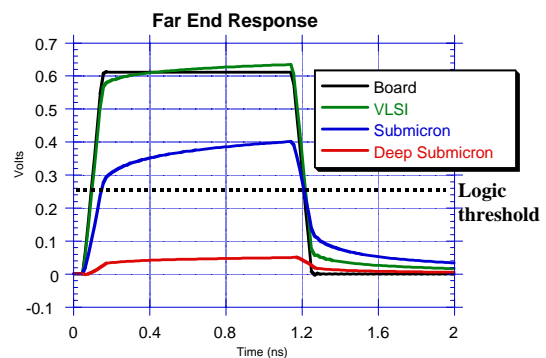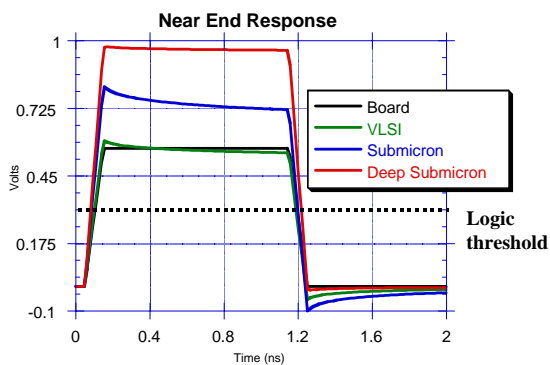length : 3 mm
near end termination: 50 Ω
far end termination 65 Ω



Interconnect Bottleneck

Signal Integrity

Crosstalk

Dispersion

Attenuation

Reflection



Distortion

Loss

Delta I Noise

Ground Bounce

Radiation

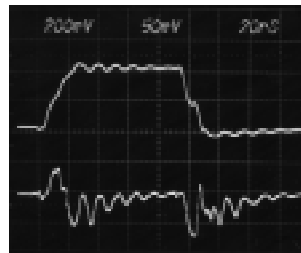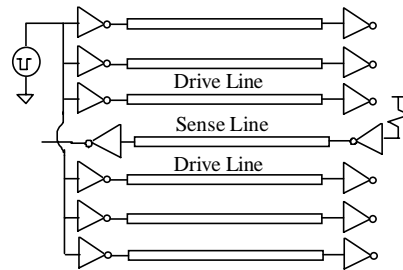


DAC 2001

© SEMCHIP

7

Mixed Signal Noise

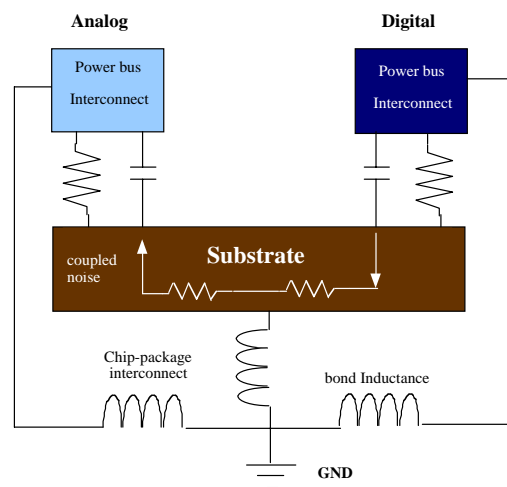


- Simultaneous switching and inductance (L_{eff})
- L_{eff} is f (current magnitude and direction)
- Interactions between noise generated by power/ground and signal paths

DAC 2001

© SEMCHIP


8

INDUCTANCE

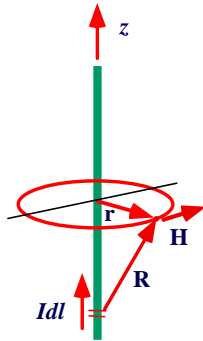

$$\text{Inductance} = \frac{\text{Total flux linked}}{\text{Current}}$$

INDUCTANCE

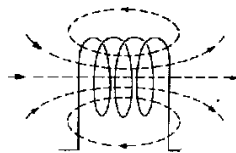


$$L = \frac{N\Phi}{I}$$

N : number of turns


Φ : flux per turn

CAPACITANCE

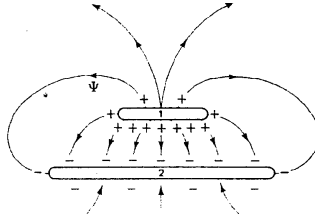

$$\text{Capacitance} = \frac{\text{Total charge}}{\text{Voltage}}$$

CAPACITANCE

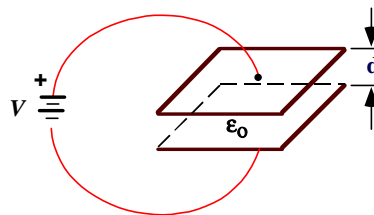

$$C = \frac{\epsilon_0 A}{d}$$

A : area

ϵ_0 : permittivity

Package Inductance & Capacitance

<u>Component</u>	<u>Capacitance</u> (pF)	<u>Inductance</u> (nH)
68 pin plastic DIP pin [†]	4	35
68 pin ceramic DIP pin ^{††}	7	20
68 pin SMT chip carrier [†]	2	7

[†] No ground plane; capacitance is dominated by wire to wire component.

^{††} With ground plane; capacitance and inductance are determined by the distance between the lead frame and the ground plane, and the lead length.

Package Inductance & Capacitance

<u>Component</u>	<u>Capacitance</u> (pF)	<u>Inductance</u> (nH)
68 pin PGA pin ^{††}	4	35
256 pin PGA pin ^{††}	7	20
Wire bond	1	1
Solder bump	0.5	0.1

[†] No ground plane; capacitance is dominated by wire to wire component.


^{††} With ground plane; capacitance and inductance are determined by the distance between the lead frame and the ground plane, and the lead length.

CONDUCTIVITY OF DIELECTRIC MATERIALS

<u>Material</u>	<u>Conductivity ($\Omega^{-1} \text{ m}^{-1}$)</u>
Germanium	2.2
Silicon	0.0016
Glass	$10^{-10} - 10^{-14}$
Quartz	0.5×10^{-17}

Loss TANGENT : $\tan\delta = \frac{\sigma}{\omega \epsilon}$


Propagation Speeds

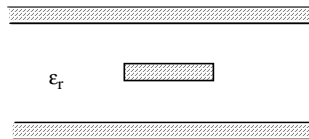


$$v = \frac{c}{\sqrt{\epsilon_r}}$$


<u>Dielectric</u>	<u>ϵ_r</u>	<u>v (cm/ns)</u>
Polymide	2.5-3.5	16-19
Silicon Dioxide	3.9	15
Epoxy Glass (PC board)	5	13
Alumina (ceramic)	9.5	10

Signal Integrity

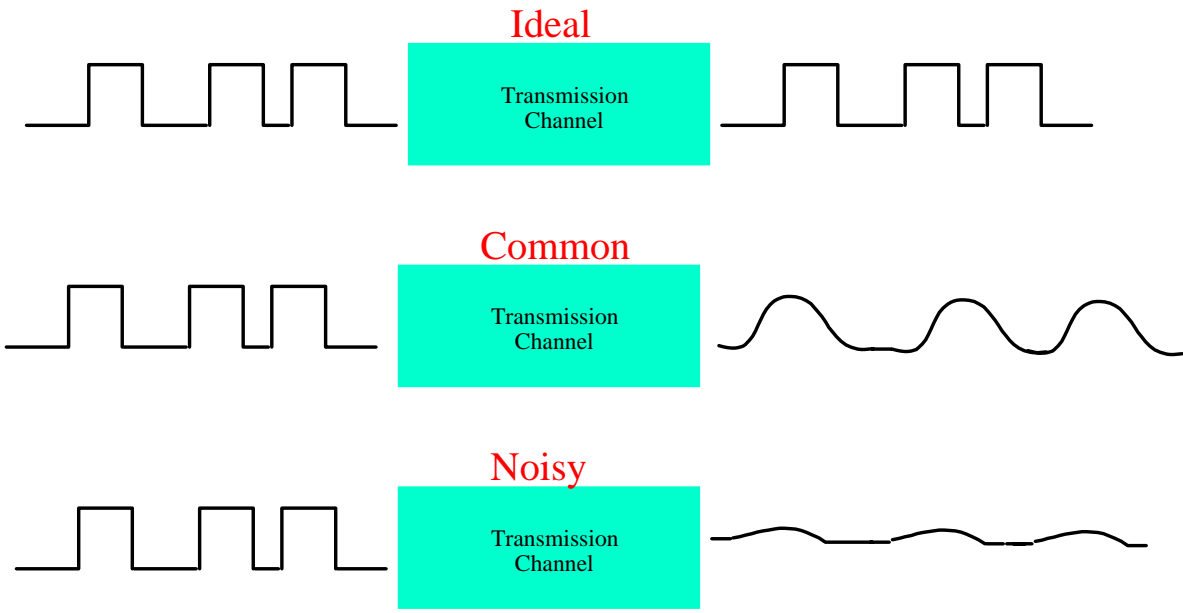


Signal Degradation

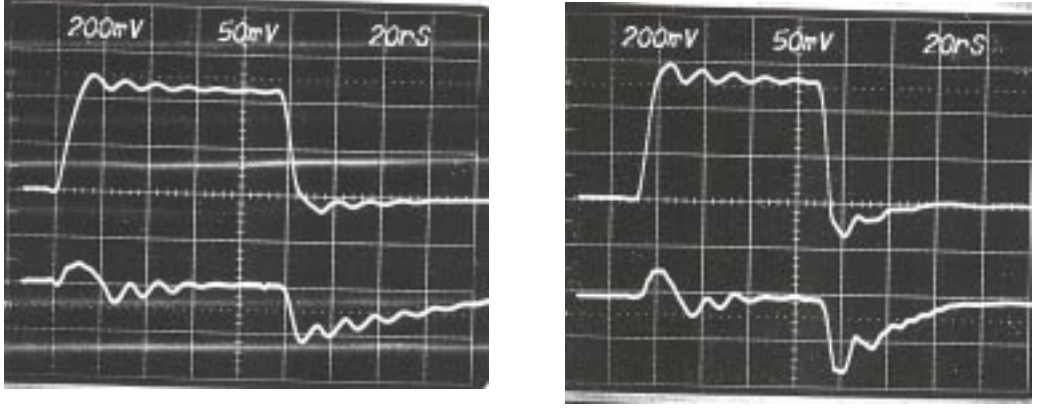


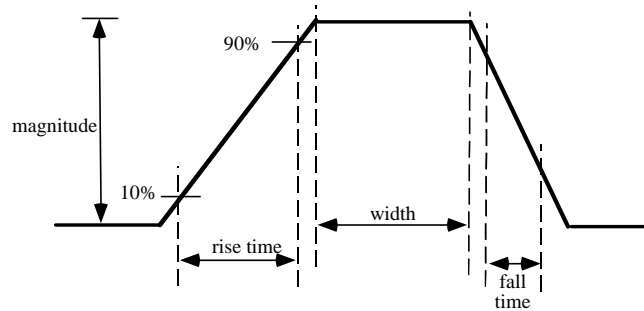

Frequency Components of Digital Signal

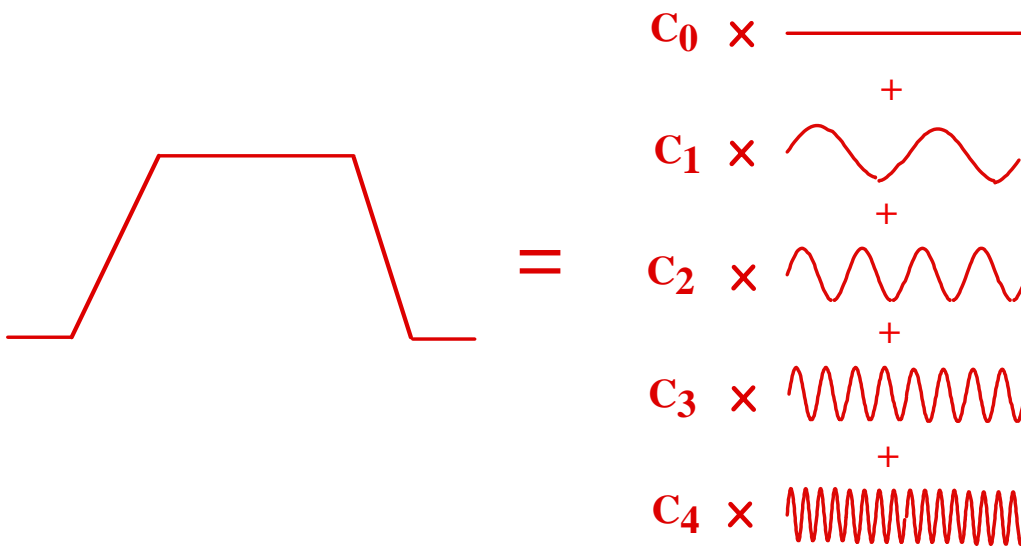

RC Network

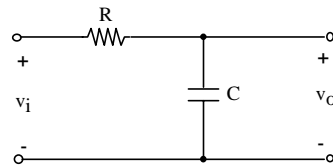


A is in the steady state gain of the network; $A = \frac{v_o(f)}{v_i(f)}$


$$|A| = \frac{1}{\sqrt{1+(f/f_2)^2}} \quad f_2 = \frac{1}{2\pi RC}$$

The gain falls to **0.707** of its low-frequency value at the frequency f_2 . f_2 is the *upper 3-dB frequency* or the **3-dB bandwidth** of the RC network.


RC Network

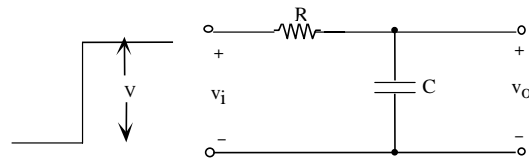

$$v_o = V(1 - e^{-t/RC})$$

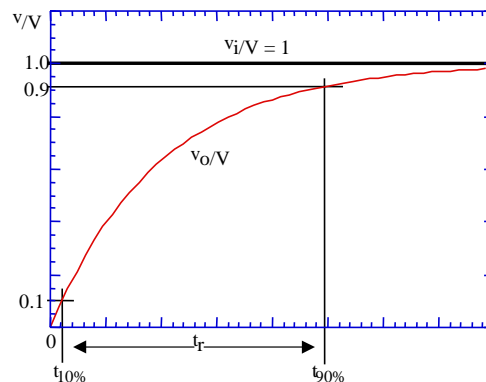

RC Network

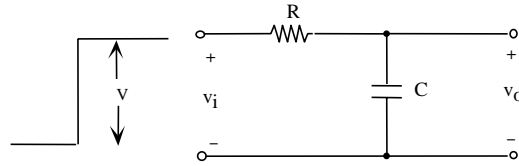


Rise time : $t_r = t_{90\%} - t_{10\%}$

$$t_r = 2.2RC = \frac{2.2}{2\pi f_2} = \frac{0.35}{f_2}$$

Rule of thumb : A 1-ns pulse
requires a circuit with a 3-dB
bandwidth of the order of 2 GHz.

WAVE PROPAGATION

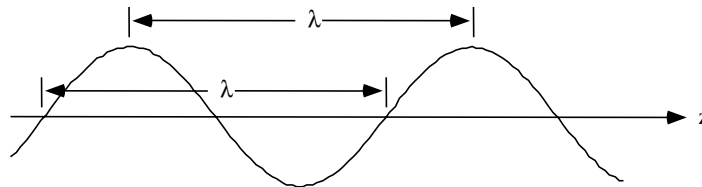

Wavelength : λ

$$\lambda = \frac{\text{propagation velocity}}{\text{frequency}}$$

Why Transmission Lines ?

In Free Space


At 10 KHz : $\lambda = 30$ km

At 10 GHz : $\lambda = 3$ cm

Transmission line behavior is prevalent when the structural dimensions of the circuits are comparable to the wavelength.


Transmission Line Model

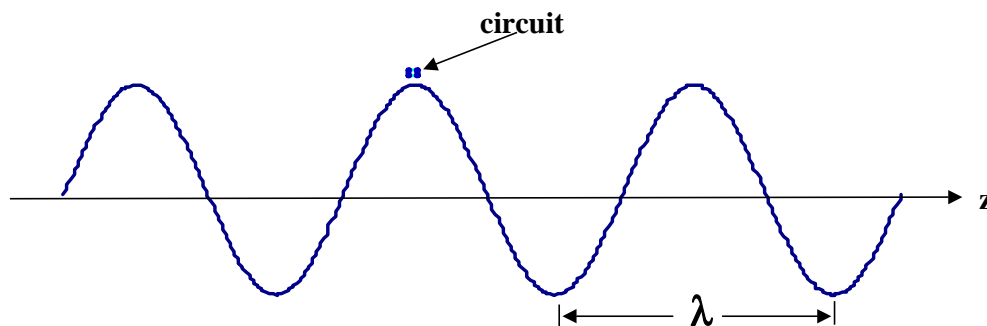Let d be the largest dimension of a circuit



If $d \ll \lambda$, a lumped model for the circuit can be used

Transmission Line Model

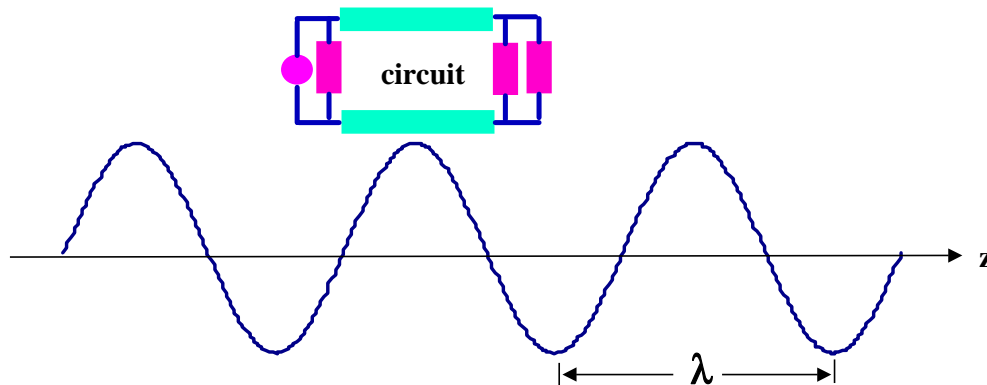

If $d \approx \lambda$, or $d > \lambda$ then use transmission line model

Frequency Dependence of Lumped Circuit Models

At higher frequencies, a lumped circuit model is no longer accurate for interconnects and one must use a distributed model. Transition frequency depends on the dimensions and relative magnitude of the interconnect parameters.

$$f \approx \frac{0.3 \times 10^9}{10d\sqrt{\epsilon_r}} \quad t_r \approx \frac{0.35}{f}$$

Lumped Circuit or Transmission Line?

A) Determine frequency or bandwidth of the signal

-Microwave: $f =$ operating frequency

-Digital: $f = \frac{0.35}{\text{rise time}}$

B) Determine propagation velocity in medium, v ,

next calculate wavelength $\lambda = \frac{v}{f}$

Lumped Circuit or Transmission Line?

C) Compare wavelength with dimensions (feature size) d .

Case 1: If $\lambda \gg d$ use lumped circuit equivalent

Total inductance = $L \times \text{length}$

Total capacitance = $C \times \text{length}$

Case 2: If $\lambda \approx 10d$ or $\lambda < 10d$, use transmission-line model

Frequency Dependence of Lumped Circuit Models

	Dimension	Frequency	Rise time
Printed circuit line (epoxy, glass)	10 in	>55 MHz	<7 ns
Package lead frame (ceramic)	1 in	>400 MHz	<0.9 ns
VLSI interconnection* (silicon)	100 μm	>8 GHz	<50 ps


* Using RC criterion for distributed effect

DAC 2001

© SEMCHIP

31


Types of Transmission Lines

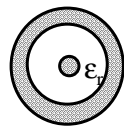


Coaxial line




Waveguide

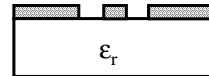


Coplanar line

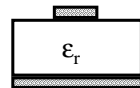

Microstrip

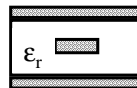

Stripline

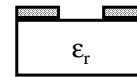


Slot line

DAC 2001

© SEMCHIP

32


Parallel-plate Transmission Line

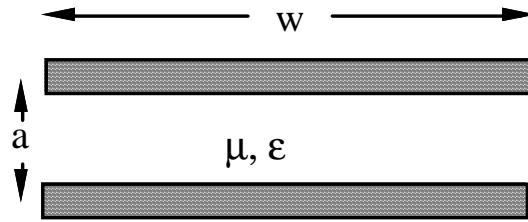

$$L = \frac{\mu a}{w}$$

$$C = \frac{\epsilon w}{a}$$


Coaxial Transmission Line

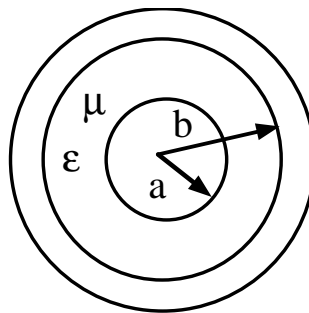


$$L = \mu \ln \frac{b}{a}$$

$$C = \frac{2\pi\epsilon}{\ln(b/a)}$$

Microstrip

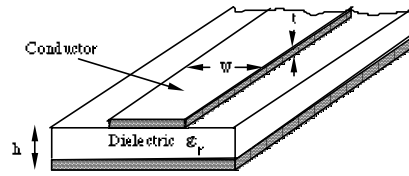


(a)

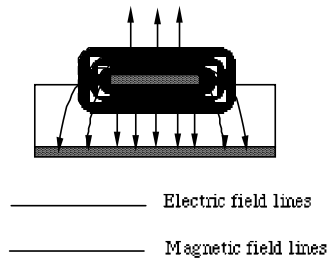

(b)


Microstrip

Microstrip Characteristic Impedance

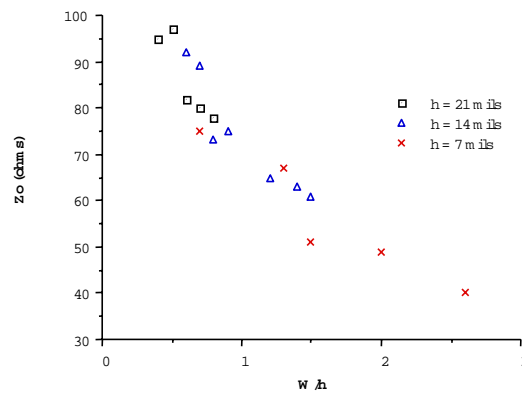


dielectric constant : 4.3.

Electric Field Configuration

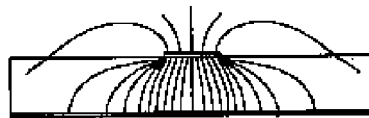



Microstrip

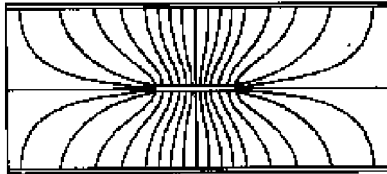


Stripline

Consequence: Wave propagation in stripline is closer to the TEM mode of propagation and the propagation of velocity is approximately $c/\sqrt{\epsilon_r}$.

TEM PROPAGATION

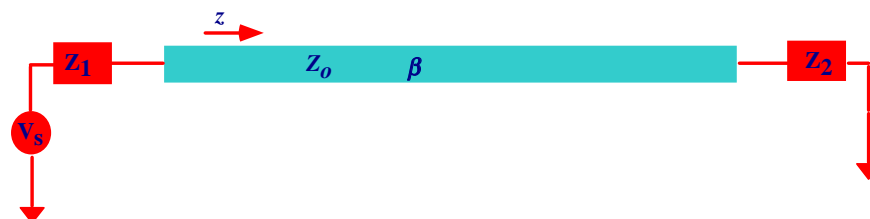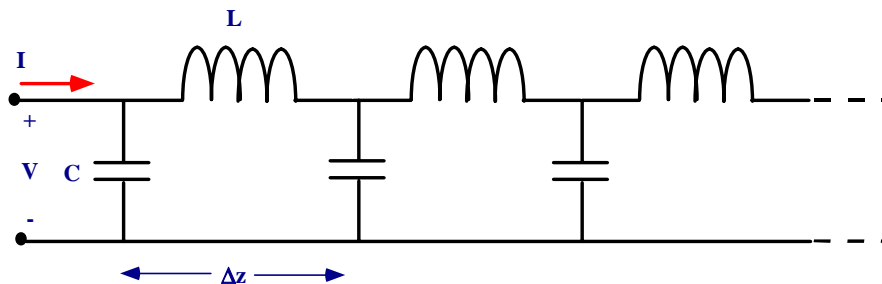

Telegrapher's Equations

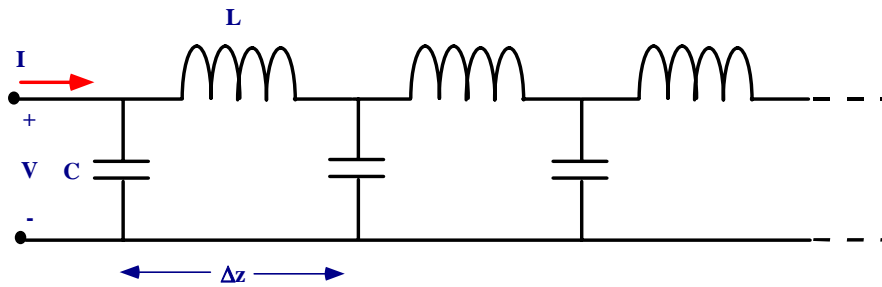


$$-\frac{\partial V}{\partial z} = L \frac{\partial I}{\partial t}$$

$$-\frac{\partial I}{\partial z} = C \frac{\partial V}{\partial t}$$


L: Inductance per unit length.

C: Capacitance per unit length.



Transmission Line Solutions

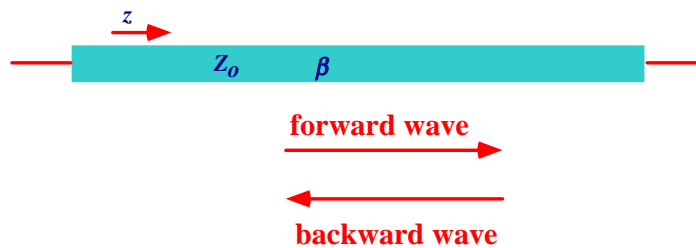


Reflection in Transmission Lines

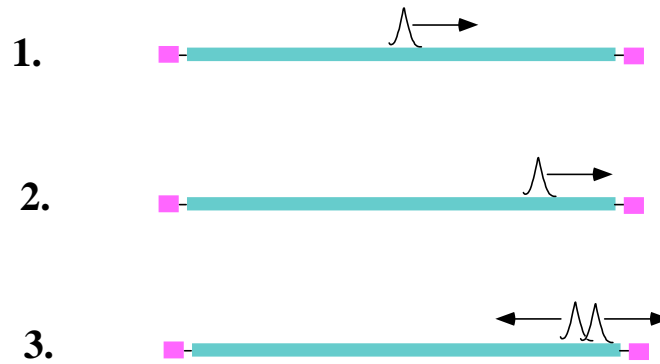

Time Domain Reflectometry

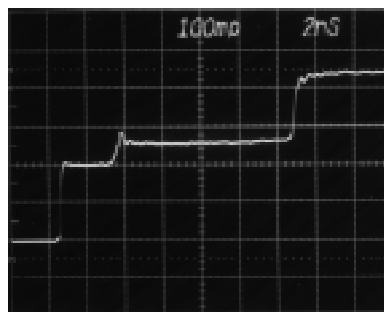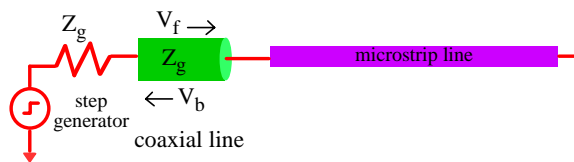

Metallic Conductors

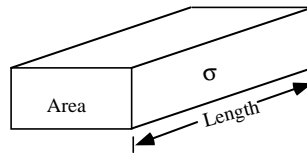

Resistance : R

$$R = \frac{\text{Length}}{\sigma \text{ Area}}$$


Package level:
W=3 mils
R=0.0045 Ω /mm

Submicron level:
W=0.25 microns
R=422 Ω /mm


Metallic Conductors

Metal	σ ($\Omega^{-1} \text{ m}^{-1} \times 10^{-7}$)
Silver	6.1
Copper	5.8
Gold	3.5
Aluminum	1.8
Tungsten	1.8
Brass	1.5
Solder	0.7


Loss in Transmission Lines

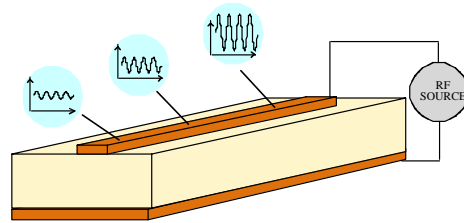

Skin Effect in Transmission Lines

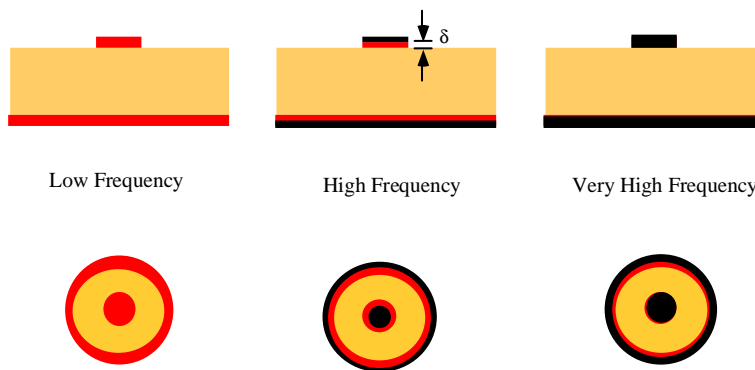

Skin Effect in Microstrip

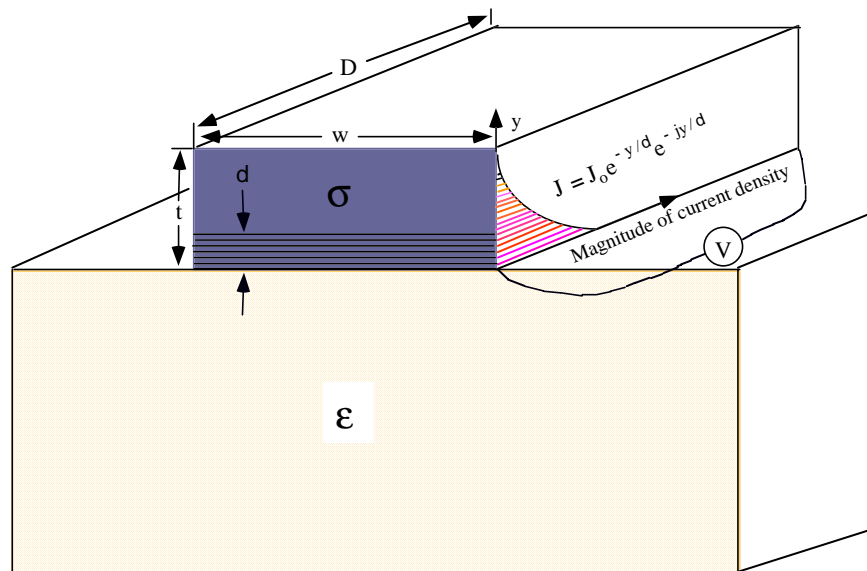

DAC 2001

© SEMCHIP

47


Skin Effect

The electric field in a material medium propagates as

$$E_0 e^{-\gamma z} = E_0 e^{-\alpha z} e^{-j\beta z}$$

where $\gamma = \alpha + j\beta$. We also have

$$\gamma = \omega \sqrt{\mu\epsilon \left(1 + j \frac{\sigma}{\omega\epsilon}\right)}$$

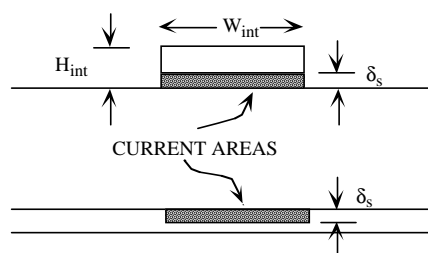


DAC 2001

© SEMCHIP

48

Lossy Transmission Line

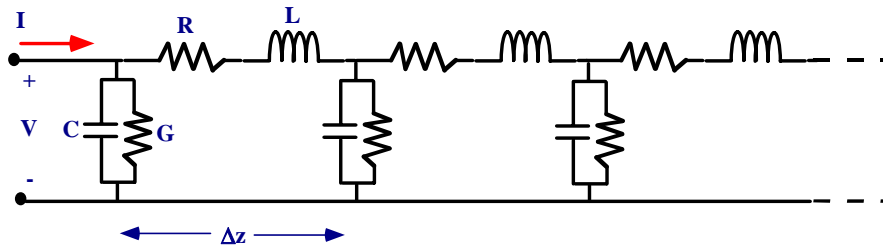

Telegraphers Equation


$$-\frac{\partial V}{\partial z} = (R + j\omega L)I = ZI$$

$$-\frac{\partial I}{\partial z} = (G + j\omega C)V = YV$$


Lossy Transmission Line



forward wave

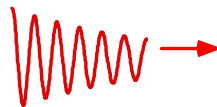

backward wave

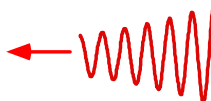

Network Analyzer







DAC 2001

© SEMCHIP

51

S Parameters of Transmission Lines

Short line

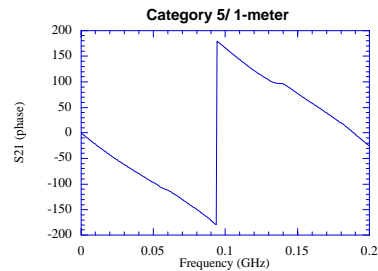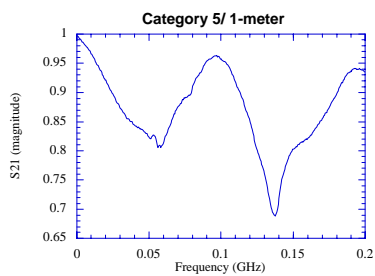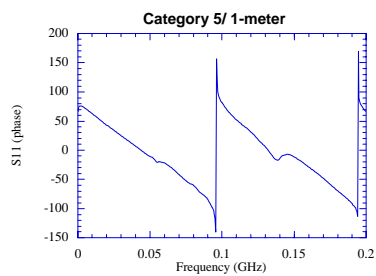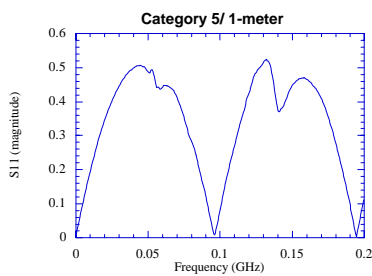


DAC 2001

© SEMCHIP

52

Two-Port Characterization

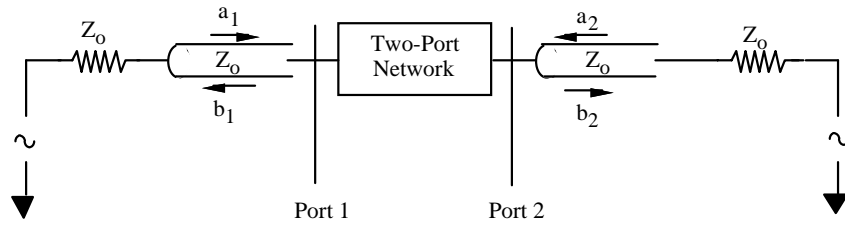

$$b_1 = S_{11} a_1 + S_{12} a_2$$

$$b_2 = S_{21} a_1 + S_{22} a_2$$

$$S_{11} = \frac{b_1}{a_1|_{a_2=0}} \quad S_{21} = \frac{b_2}{a_1|_{a_2=0}}$$

$$S_{12} = \frac{b_1}{a_2|_{a_1=0}} \quad S_{22} = \frac{b_2}{a_2|_{a_1=0}}$$



DAC 2001

© SEMCHIP

53

Microstrip Characterization

- Network analyzer measurement of S parameters
- Use de-embedding scheme
- Use extraction algorithm


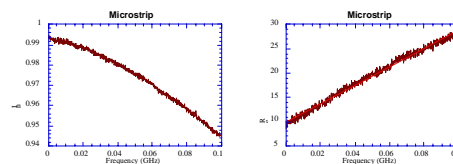
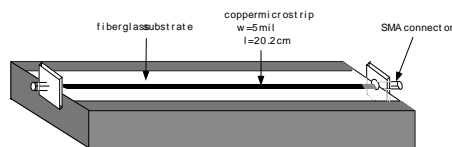


DAC 2001

© SEMCHIP

54

Package Level Characterization

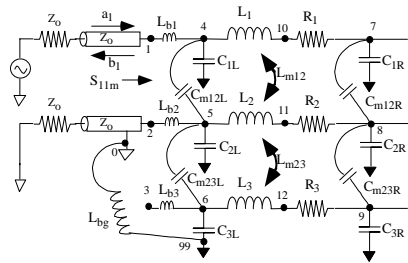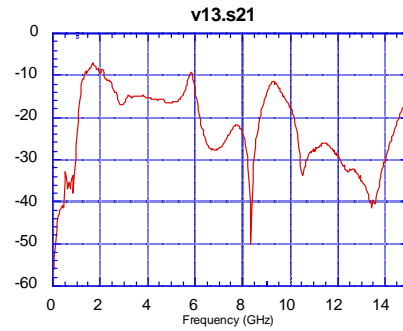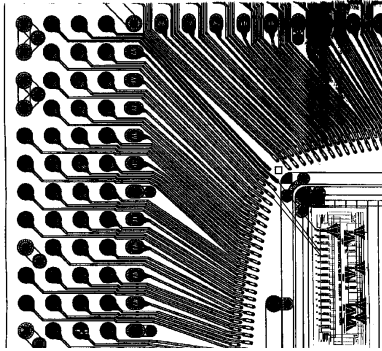

DAC 2001

© SEMCHIP

55

Crosstalk Noise and Coupled Transmission Lines

José Schutt-Ainé
SemChip

DAC Tutorial


22, June 2001

DAC 2001

© SEMCHIP

56

TEM PROPAGATION

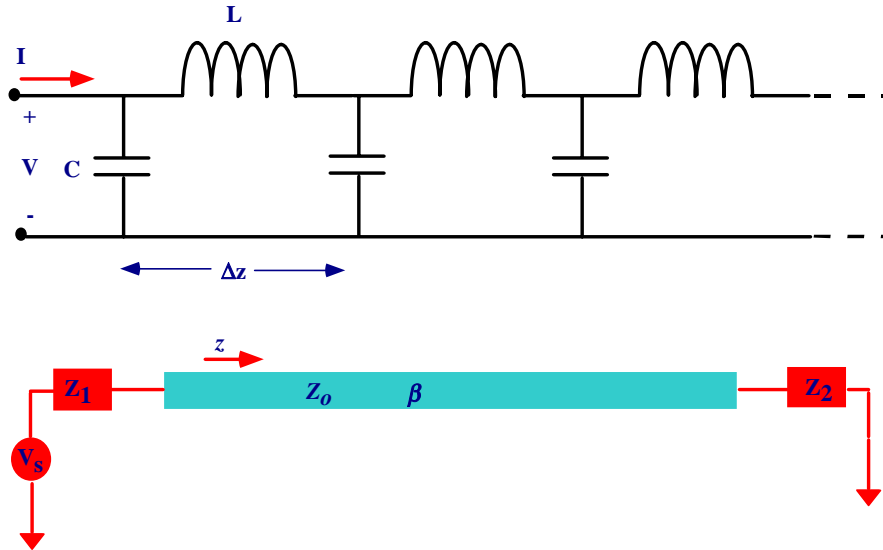


DAC 2001

© SEMCHIP

57

Telegrapher's Equations

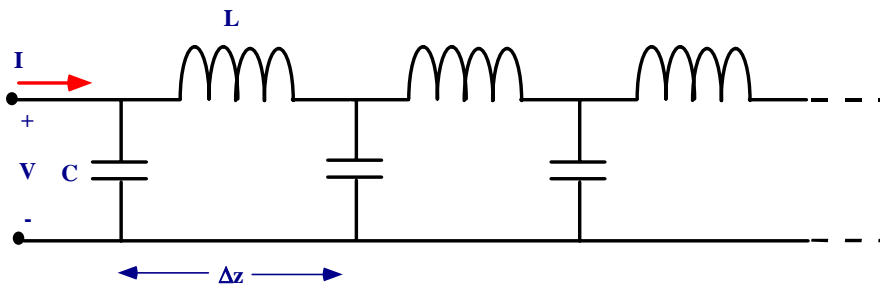

$$-\frac{\partial V}{\partial z} = L \frac{\partial I}{\partial t}$$

$$-\frac{\partial I}{\partial z} = C \frac{\partial V}{\partial t}$$

L: Inductance per unit length.


C: Capacitance per unit length.

DAC 2001

© SEMCHIP

58



Crosstalk and Coupled Line Analysis

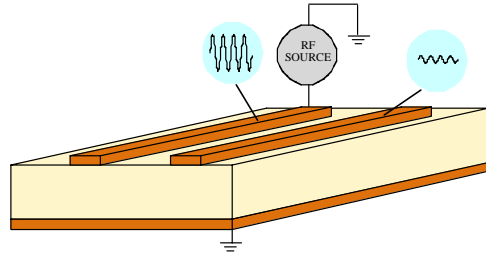





Crosstalk Noise

Signal Integrity

- | | | |
|----------------------|----------------------|--------------------|
| Crosstalk | Dispersion | Attenuation |
| Reflection | Distortion | Loss |
| Delta I Noise | Ground Bounce | Radiation |

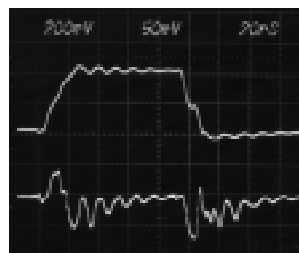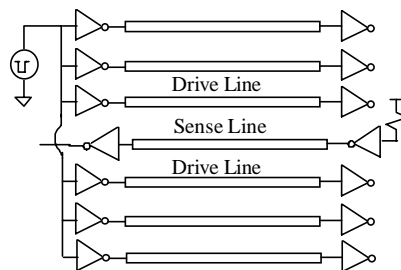

Crosstalk noise depends on termination

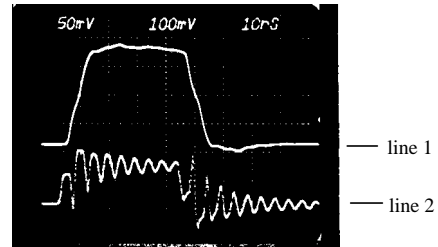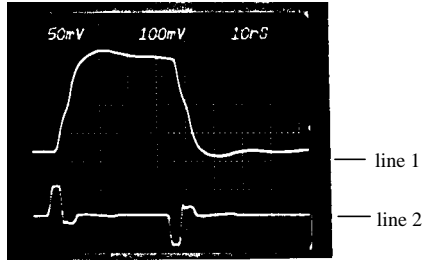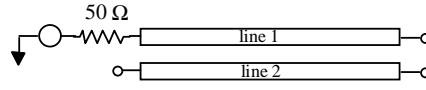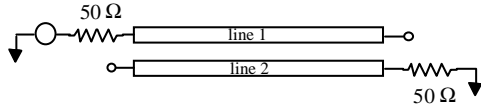


DAC 2001


© SEMCHIP

61


Crosstalk depends on signal rise time

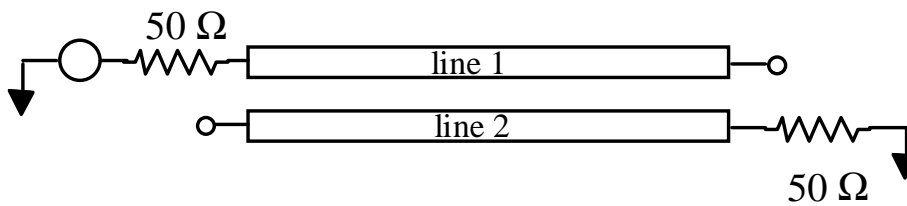

$t_r = 1\ \text{ns}$

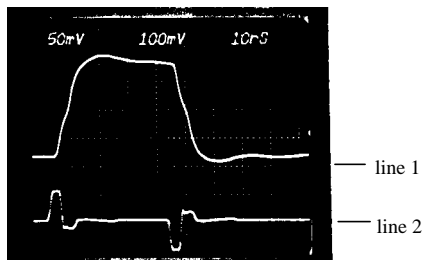

$t_r = 7\ \text{ns}$

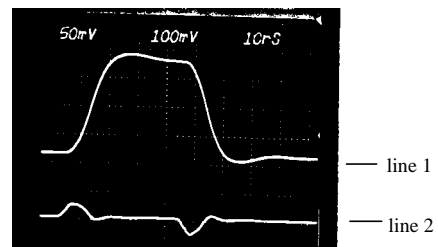


DAC 2001


© SEMCHIP

62


Crosstalk depends on signal rise time

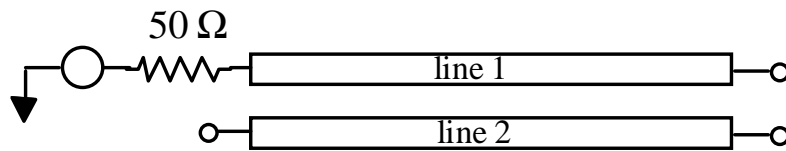



$t_r = 1\ \text{ns}$

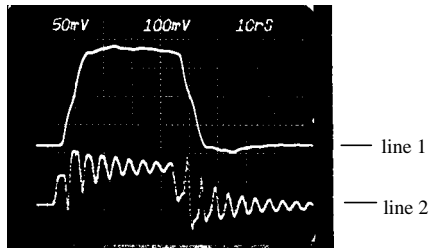

$t_r = 7\ \text{ns}$

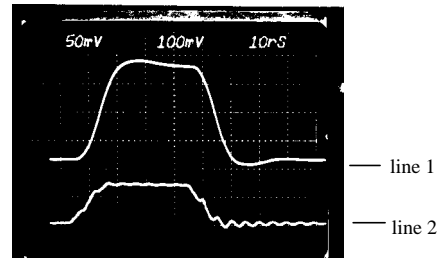

Coupled Transmission Lines

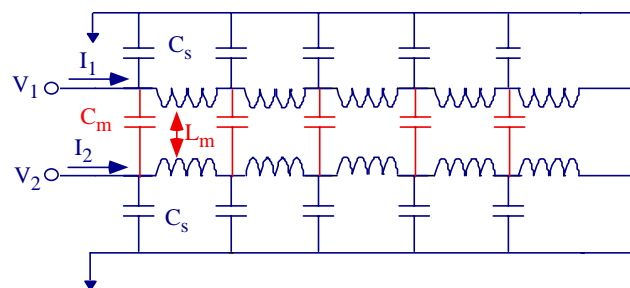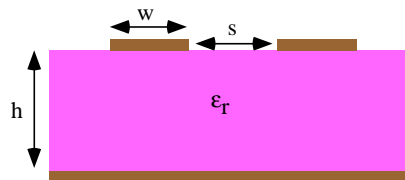

Telegraphers Equations for Coupled Transmission Lines

Maxwellian Form

$$-\frac{\partial V_1}{\partial z} = L_{11} \frac{\partial I_1}{\partial t} + L_{12} \frac{\partial I_2}{\partial t}$$

$$-\frac{\partial V_2}{\partial z} = L_{21} \frac{\partial I_1}{\partial t} + L_{22} \frac{\partial I_2}{\partial t}$$

$$-\frac{\partial I_1}{\partial z} = C_{11} \frac{\partial V_1}{\partial t} + C_{12} \frac{\partial V_2}{\partial t}$$

$$-\frac{\partial I_2}{\partial z} = C_{21} \frac{\partial V_1}{\partial t} + C_{22} \frac{\partial V_2}{\partial t}$$

Telegraphers Equations for Coupled Transmission Lines

Physical form

$$-\frac{\partial V_1}{\partial z} = L_s \frac{\partial I_1}{\partial t} + L_m \frac{\partial I_2}{\partial t}$$

$$-\frac{\partial V_2}{\partial z} = L_m \frac{\partial I_1}{\partial t} + L_s \frac{\partial I_2}{\partial t}$$

$$-\frac{\partial I_1}{\partial z} = C_s \frac{\partial V_1}{\partial t} + C_m \frac{\partial V_1}{\partial t} - C_m \frac{\partial V_2}{\partial t}$$

$$-\frac{\partial I_2}{\partial z} = -C_m \frac{\partial V_1}{\partial t} + C_m \frac{\partial V_2}{\partial t} + C_s \frac{\partial V_2}{\partial t}$$

Relations Between Physical and Maxwellian Parameters

$$L_{11} = L_{22} = L_s$$

$$L_{12} = L_{21} = L_m$$

$$C_{11} = C_{22} = C_s + C_m$$

$$C_{12} = C_{21} = -C_m$$

Even Mode

$$-\frac{\partial V_e}{\partial z} = (L_{11} + L_{12}) \frac{\partial I_e}{\partial t}$$

**Add voltage
and current
equations**

$$-\frac{\partial I_e}{\partial z} = (C_{11} + C_{12}) \frac{\partial V_e}{\partial t}$$

V_e : Even mode voltage $V_e = \frac{1}{2}(V_1 + V_2)$

I_e : Even mode current $I_e = \frac{1}{2}(I_1 + I_2)$

$$Z_e = \sqrt{\frac{L_{11} + L_{12}}{C_{11} + C_{12}}} = \sqrt{\frac{L_s + L_m}{C_s}}$$

Impedance

$$v_e = \frac{1}{\sqrt{(L_{11} + L_{12})(C_{11} + C_{12})}} = \frac{1}{\sqrt{(L_s + L_m)C_s}}$$

velocity

Odd Mode

$$-\frac{\partial V_d}{\partial z} = (L_{11} - L_{12}) \frac{\partial I_d}{\partial t}$$

$$-\frac{\partial I_d}{\partial z} = (C_{11} - C_{12}) \frac{\partial I_d}{\partial t}$$

**Subtract voltage
and current
equations**

V_d : Odd mode voltage

$$V_d = \frac{1}{2}(V_1 - V_2)$$

I_d : Odd mode current

$$I_d = \frac{1}{2}(I_1 - I_2)$$


$$Z_d = \sqrt{\frac{L_{11} - L_{12}}{C_{11} - C_{12}}} = \sqrt{\frac{L_s - L_m}{C_s + 2C_m}}$$

Impedance

$$v_d = \frac{1}{\sqrt{(L_{11} - L_{12})(C_{11} - C_{12})}} = \frac{1}{\sqrt{(L_s - L_m)(C_s + 2C_m)}}$$

velocity

Even Mode

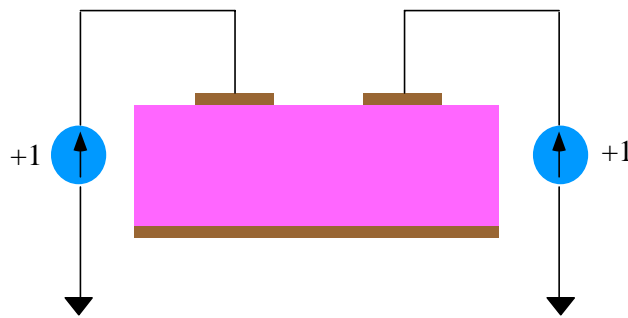


$$Z_e = \sqrt{\frac{L_s + L_m}{C_s}}$$

Impedance

$$v_e = \frac{1}{\sqrt{(L_s + L_m)C_s}}$$

velocity

Odd Mode

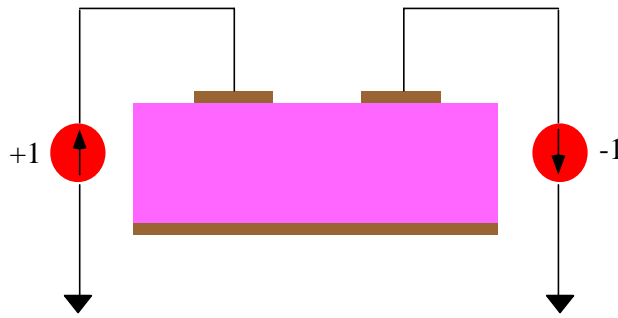

$$Z_d = \sqrt{\frac{L_s - L_m}{C_s + 2C_m}}$$

Impedance

$$v_d = \frac{1}{\sqrt{(L_s - L_m)(C_s + 2C_m)}}$$

velocity

PHYSICAL SIGNIFICANCE OF EVEN- AND ODD-MODE IMPEDANCES

- * Z_e and Z_d are the wave resistance seen by the even and odd mode travelling signals respectively.
- * The impedance of each line is no longer described by a single characteristic impedance; instead, we have

$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2$$

EVEN AND ODD-MODE IMPEDANCES


Z_{11}, Z_{22} : Self Impedances

Z_{12}, Z_{21} : Mutual Impedances

For symmetrical lines,

$Z_{11} = Z_{22}$ and $Z_{12} = Z_{21}$


EXAMPLE (Microstrip)

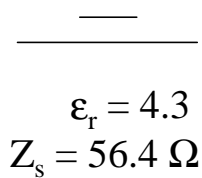

Single Line

Dielectric height = 6 mils

Width = 8 mils

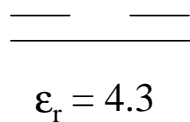

Coupled Lines


Height = 6 mils

Width = 8 mils

Spacing = 12 mils

$$\begin{aligned} Z_e &= 68.1 \Omega & Z_d &= 40.8 \Omega \\ Z_{11} &= 54.4 \Omega & Z_{12} &= 13.6 \Omega \end{aligned}$$

Even Mode

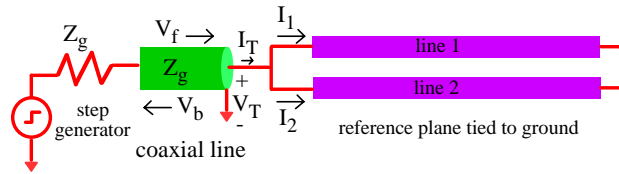


$$I_{tdr} = \left[\frac{a_e(t,0)}{Z_e} + \frac{a_d(t,0)}{Z_d} \right] + \left[\frac{a_e(t,0)}{Z_e} - \frac{a_d(t,0)}{Z_d} \right]$$

$$V_{tdr} = a_e(t,0) - a_d(t,0) \quad a_d(t,0) = 0$$

$$\frac{V_{tdr}}{I_{tdr}} = \frac{Z_e}{2} \quad Z_e = 2 \left(\frac{1 + \rho_e}{1 - \rho_e} \right) Z_g \quad v_e = \frac{2l}{\tau_e}$$

Odd Mode

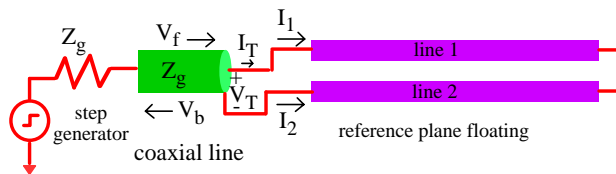

$$V_{tdr} = a_e(t,0) + a_d(t,0) - [a_e(t,0) - a_d(t,0)] = V_f + V_b$$

$$I_{tdr} = \left[\frac{a_e(t,0)}{Z_e} + \frac{a_d(t,0)}{Z_d} \right] \quad I_{tdr} = - \left[\frac{a_e(t,0)}{Z_e} - \frac{a_d(t,0)}{Z_d} \right]$$

$$a_e(t,0) = 0, \quad \frac{V_{tdr}}{I_{tdr}} = 2Z_d$$

$$Z_d = \frac{1}{2} \left(\frac{1 + \rho_d}{1 - \rho_d} \right) Z_g, \quad v_d = \frac{2l}{\tau_d}$$

EXTRACT INDUCTANCE AND CAPACITANCE COEFFICIENTS

$$L_s = \frac{1}{2} \left[\frac{Z_e}{v_e} + \frac{Z_d}{v_d} \right]$$


$$C_s = \frac{1}{Z_e v_e}$$

$$L_m = \frac{1}{2} \left[\frac{Z_e}{v_e} - \frac{Z_d}{v_d} \right]$$


$$C_m = \frac{1}{2} \left[\frac{1}{Z_e v_e} - \frac{1}{Z_d v_d} \right]$$

$$Z_d < Z_s < Z_e$$


Measured even-mode impedance

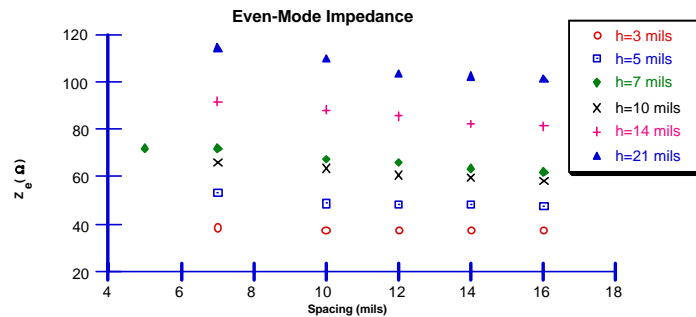


Measured odd-mode impedance

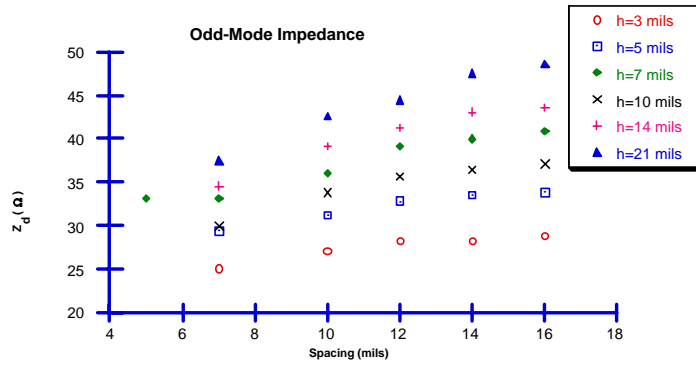


Measured even-mode velocity

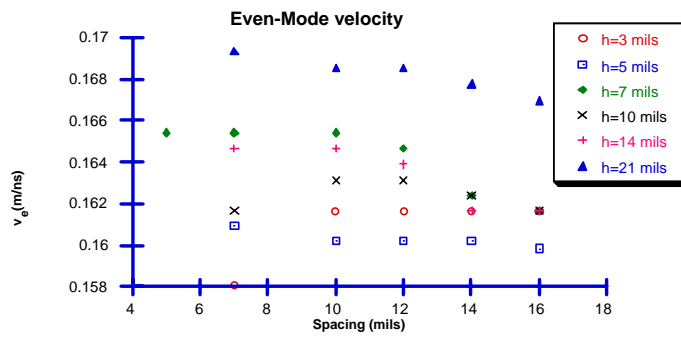


Measured odd-mode velocity

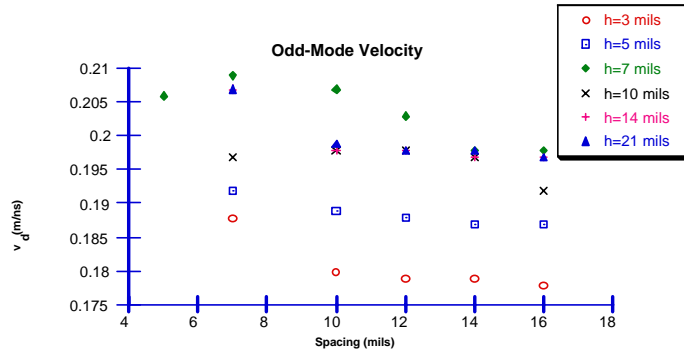


Measured mutual inductance

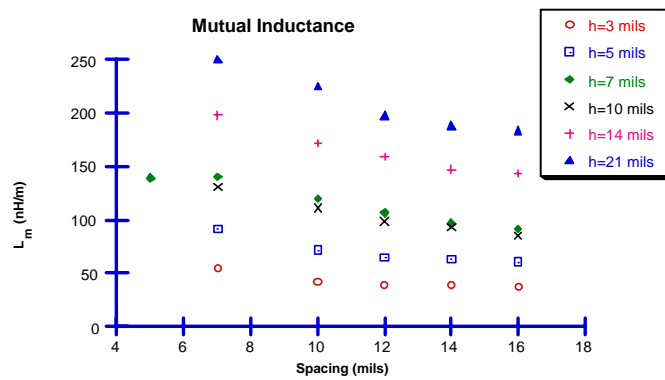


Measured mutual capacitance

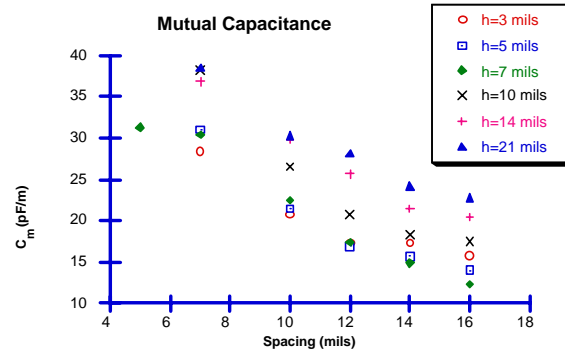

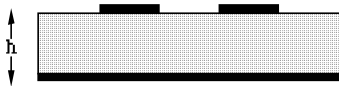Modal Velocities in Stripline and Microstrip




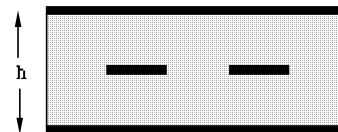Microstrip : Inhomogeneous structure, odd and even-mode velocities must have different values.



Stripline : Homogeneous configuration, odd and even-mode velocities have approximately the same values.

Microstrip vs Stripline

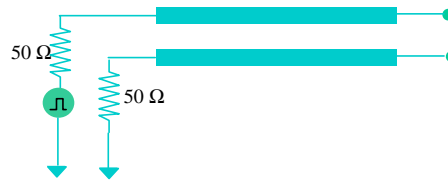


Microstrip (h = 8 mils)

$w = 8$ mils
 $\epsilon_r = 4.32$
 $L_s = 377$ nH/m
 $C_s = 82$ pF/m
 $L_m = 131$ nH/m
 $C_m = 23$ pF/m
 $v_e = 0.155$ m/ns
 $v_d = 0.178$ m/ns



Stripline (h = 16 mils)

$w = 8$ mils
 $\epsilon_r = 4.32$
 $L_s = 466$ nH/m
 $C_s = 86$ pF/m
 $L_m = 109$ nH/m
 $C_m = 26$ pF/m
 $v_e = 0.142$ m/ns
 $v_d = 0.142$ m/ns


Microstrip vs Stripline

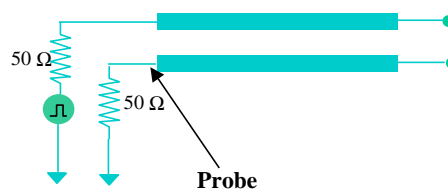

Sense line response at near end

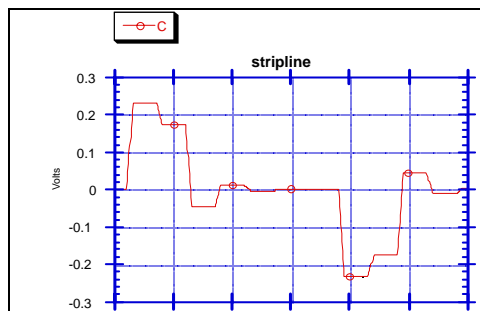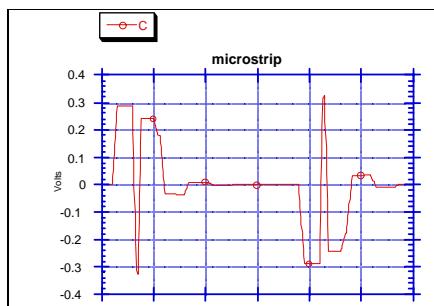


General Solution for Voltages

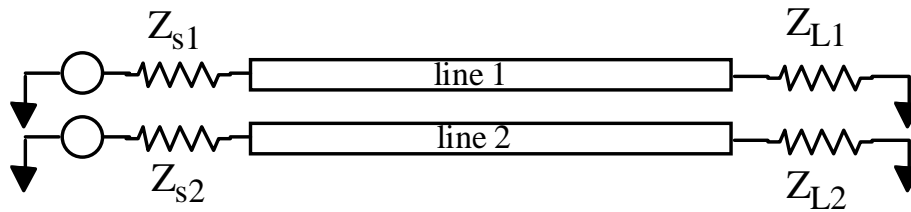

$$V_1(z) = \underbrace{A_e e^{-\frac{j\omega z}{v_e}} + B_e e^{+\frac{j\omega z}{v_e}}}_{\text{even}} + \underbrace{A_d e^{-\frac{j\omega z}{v_d}} + B_d e^{+\frac{j\omega z}{v_d}}}_{\text{odd}}$$

$$V_2(z) = \underbrace{A_e e^{-\frac{j\omega z}{v_e}} + B_e e^{+\frac{j\omega z}{v_e}}}_{\text{even}} - \underbrace{A_d e^{-\frac{j\omega z}{v_d}} - B_d e^{+\frac{j\omega z}{v_d}}}_{\text{odd}}$$



General Solution for Currents

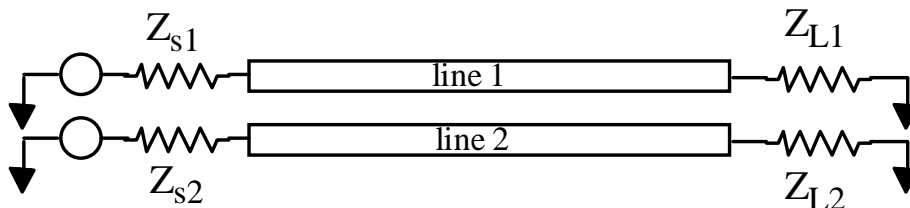



$$I_1(z) = \frac{1}{Z_e} \left[\underbrace{A_e e^{-\frac{j\omega z}{v_e}} - B_e e^{+\frac{j\omega z}{v_e}}}_{\text{even}} \right] + \frac{1}{Z_d} \left[\underbrace{A_d e^{-\frac{j\omega z}{v_d}} - B_d e^{+\frac{j\omega z}{v_d}}}_{\text{odd}} \right]$$






$$I_2(z) = \frac{1}{Z_e} \left[\underbrace{A_e e^{-\frac{j\omega z}{v_e}} - B_e e^{+\frac{j\omega z}{v_e}}}_{\text{even}} \right] - \frac{1}{Z_d} \left[\underbrace{A_d e^{-\frac{j\omega z}{v_d}} - B_d e^{+\frac{j\omega z}{v_d}}}_{\text{odd}} \right]$$

Coupling of Modes (asymmetric load)

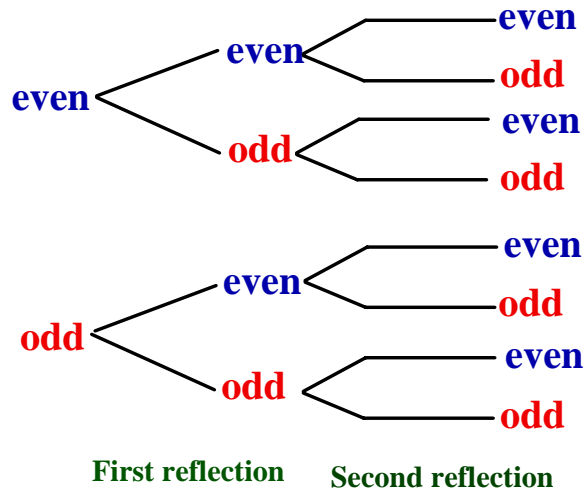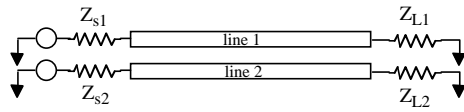


Coupling of Modes (symmetric load)

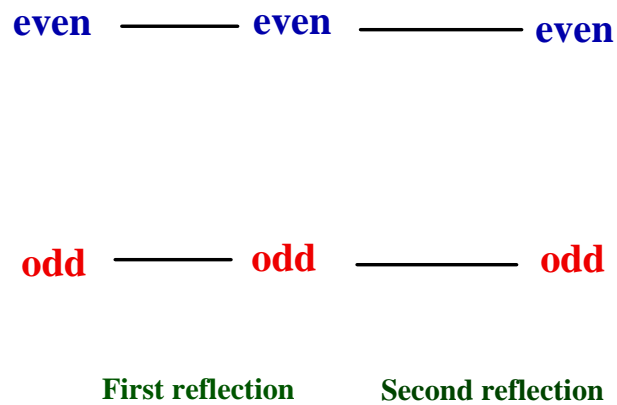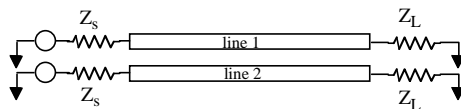

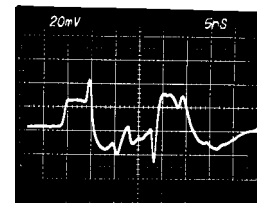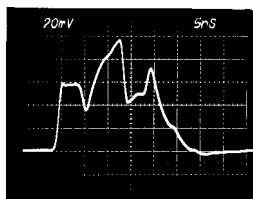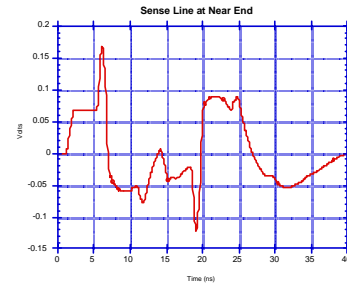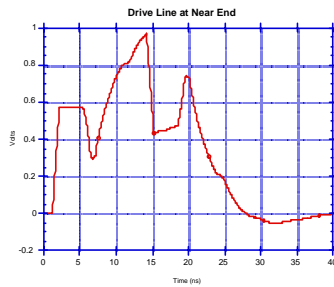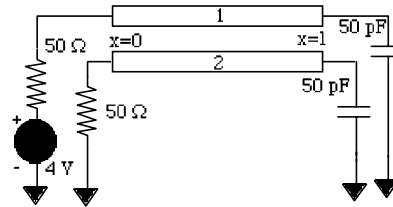

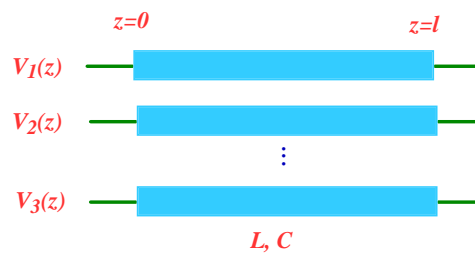TELGRAPHER'S EQUATION FOR N COUPLED TRANSMISSION LINES




$$-\frac{\partial V}{\partial z} = L \frac{\partial I}{\partial t}$$

$$-\frac{\partial I}{\partial z} = C \frac{\partial V}{\partial t}$$

V and I are the line voltage and line current VECTORS respectively (dimension n).


N-LINE SYSTEM

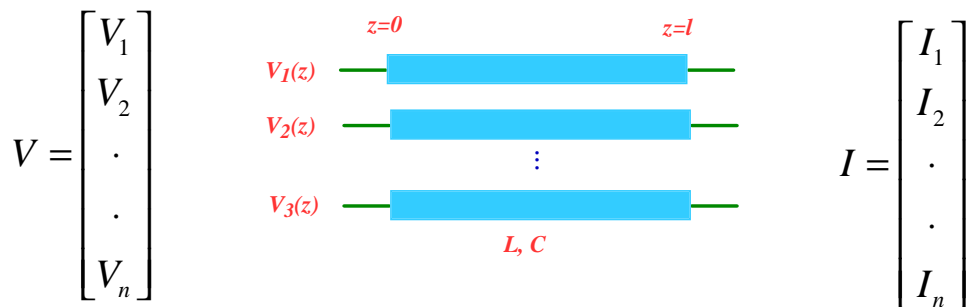

L and C are the inductance and capacitance MATRICES respectively

$$L = \begin{bmatrix} L_{11} & L_{12} & \cdot & \cdot \\ L_{21} & L_{22} & \cdot & \cdot \\ \cdot & \cdot & \cdot & \cdot \\ \cdot & \cdot & \cdot & L_{nn} \end{bmatrix} \quad C = \begin{bmatrix} C_{11} & C_{12} & \cdot & \cdot \\ C_{21} & C_{22} & \cdot & \cdot \\ \cdot & \cdot & \cdot & \cdot \\ \cdot & \cdot & \cdot & C_{nn} \end{bmatrix}$$

COUPLED LOSSY TRANSMISSION LINES

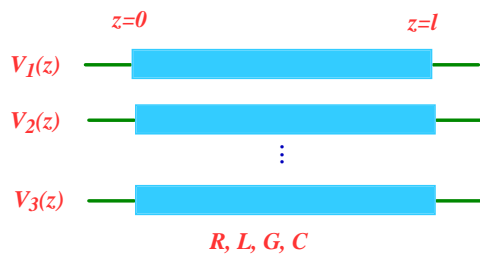


Time Domain

$$-\frac{\partial V}{\partial z} = RI + L \frac{\partial I}{\partial t}$$

$$-\frac{\partial I}{\partial z} = GV + C \frac{\partial V}{\partial t}$$

COUPLED LOSSY TRANSMISSION LINES

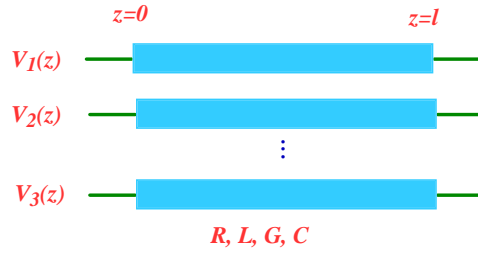

Frequency Domain


$$-\frac{\partial V}{\partial z} = ZI$$

$$-\frac{\partial I}{\partial z} = YV$$

$$Z = R + j\omega L$$

$$Y = G + j\omega C$$





7-Line Coupled-Microstrip System

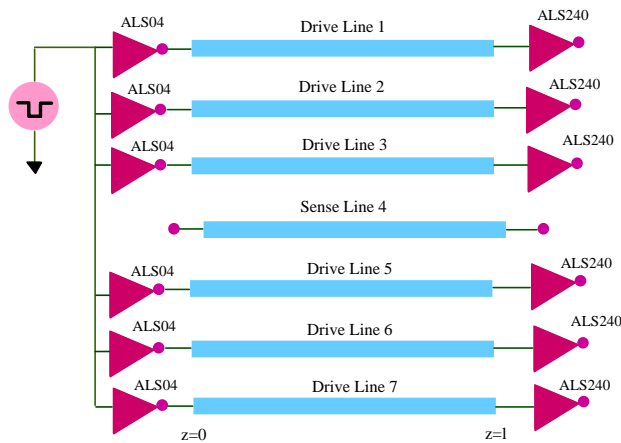

$$L_s = 312 \text{ nH/m}; \quad C_s = 100 \text{ pF/m};$$

$$L_m = 85 \text{ nH/m}; \quad C_m = 12 \text{ pF/m}.$$

Drive Line 3

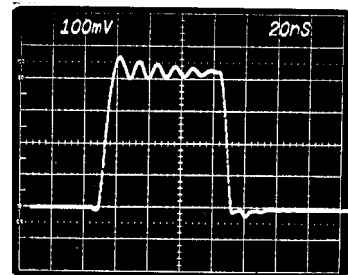
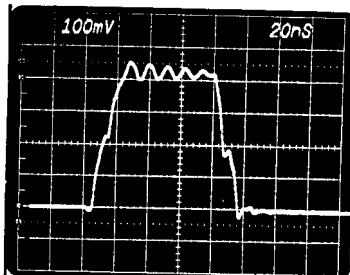
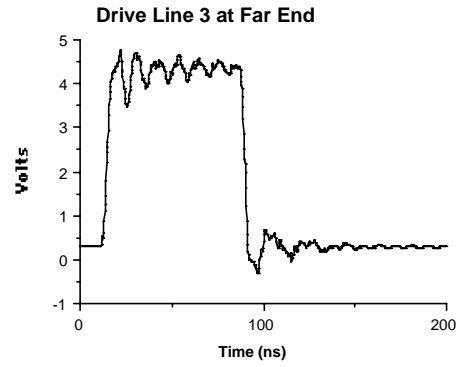
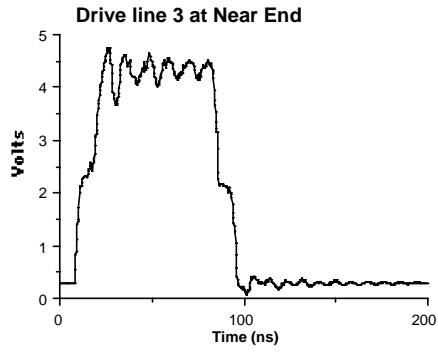


DAC 2001

© SEMCHIP

97

Sense Line

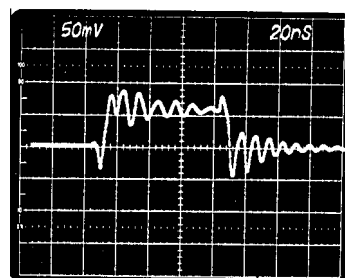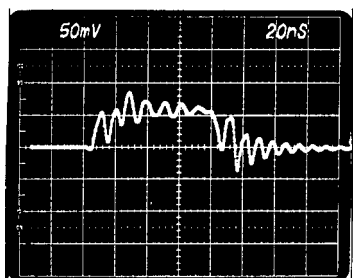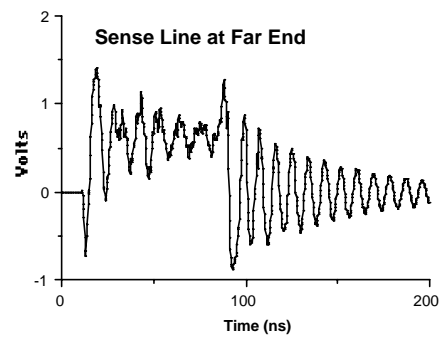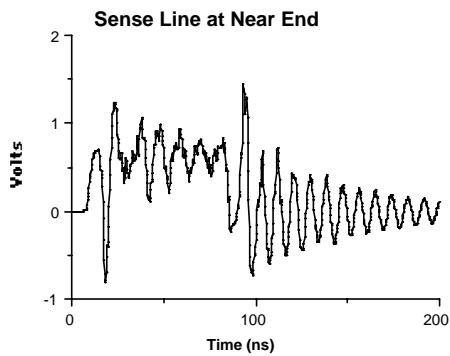

DAC 2001

© SEMCHIP

98